



*Agnel Charities'*

## Fr. C. RODRIGUES INSTITUTE OF TECHNOLOGY

DEPARTMENT: Electronics and Telecommunication Engineering.

### LABORATORY CONTINUOUS ASSESSMENT FORMAT

First /Second Half of 2022

**Course Name:** Principles of Communication Engineering Lab (ECL403)

**Name of the Teacher:** Prof. Sadhana Pai

**Name of the Student:** Rishi Raturi

**Roll No:** 3020148

**Semester:** IV

**Batch:** 2nd

**Practical No:** 2

**Date of Practical:** 25-01-2022

**Date of Report Submission:** 04-02-2022

**Title:** Amplitude modulation

**Course Outcome:** Perform an experiment to design circuits and demonstrate amplitude modulation and demodulation


### ASSESSMENT

Sr. No.	Parameter for Assessment	Marks	Rubrics		
1.	<b>Practical Performance / Active Participation (03Marks)</b>		Above Average (03)	Average (02)	Below Average (01)
2.	<b>Report Presentation (02 Marks)</b>		Above Average (02)	Average (01)	Below Average (00)
3.	<b>Understanding (03 Marks)</b>		Above Average (03)	Average (02)	Below Average (01)
4.	<b>Regularity in Submission (02 Marks)</b>		Timely (02)	Late (01) ( $\leq 2$ Weeks from the date of Practical)	Very Late (00) ( $> 2$ Weeks from the date of Practical)

**Total Marks (10):**

**Teacher's Signature:**

**Date:**

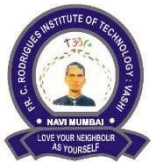

**Fr.C.Rodrigues Institute of Technology, Vashi Dept. of  
Electronics and Telecommunication Engineering. IV SEM  
EXTC**

**SUB: Principles of Communication Engg. Lab**

**AM DETECTION**


<b>Expt No.</b>	2	<b>Date: 25-01-2022</b>
<b>AIM</b>	To Simulate amplitude demodulation using diode	
<b>SOFTWARE TOOL</b>	LTSpice software	
<b>THEORY</b>	Write about: Working of the circuit used.	

Theory


Date 04.02.2022

### 1. Amplitude Detection:

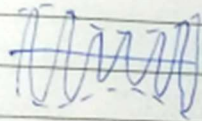
- (1) The process of Amplitude detection is also called as Amplitude 'Demodulation'.
- (2) Demodulation is exactly the opposite process of modulation.
- (3) The original modulating signal is recovered back from the AM signal by the process of detection.
- (4) Thus the process of detection or demodulation is the process of recovering the message signal from the received modulated signal.



AM wave

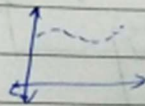

original message signal.

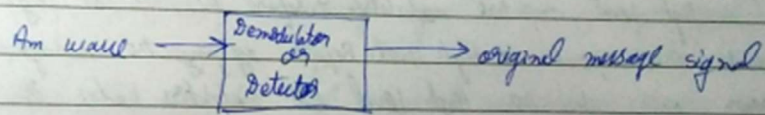

There are two types


- (1) Square law detector
- (2) Envelope detector.


### Working of circuit:

- Here our circuit consists of differential amplifier. Here this is provided with modulating signal of 3V amplitude and frequency of 1kHz is given and superimposed on the carrier signal of amplitude 1V and frequency of 100kHz.
- The output of opamp is connected to RLC circuit which acts as a filter.
- This filters out the unwanted signal and expected o/p (AM signal) is obtained.
- After that, AM signal is sent as i/p to develop a detector, which consists of an ideal diode, a capacitor and a resistor.
- The detected signal o/p is obtained at the resistor and

## PROCEDURE

1. Click on 'File' on menu bar and click on 'New Schematic' to get schematic window.
2. For AM generation use the circuit tested in Expt No. 1
3. Get the components and place them as shown in the given circuit diagram.
4. Connect the components using 'wire' tool.
5. Connect the output of the AM generator as input to the envelop detector.

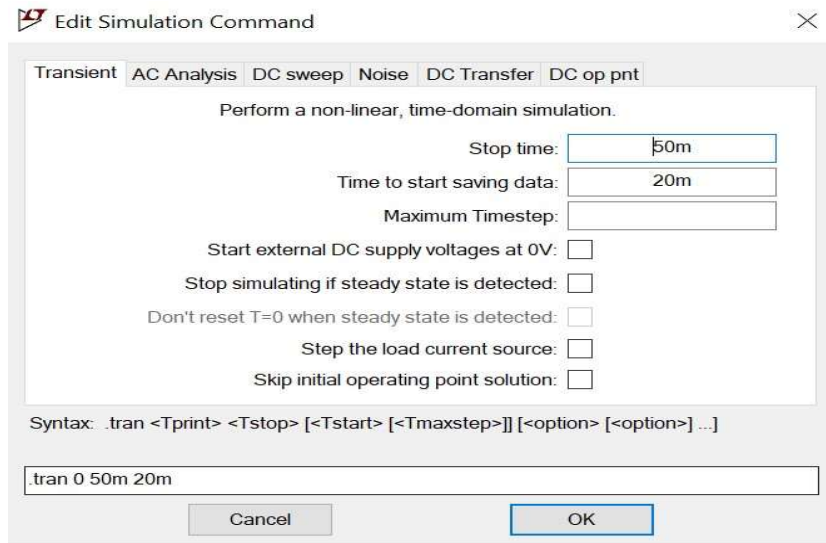6. Simulate using  Run. Following window appears. Click on 'Transient' and set the values as shown.




7. Click on 'Run' again. Wait till the output window appears.
8. Observe AM signal and diode detector output signal FFT of demodulated signal.
9. Vary the input and note down Detector output
10. Vary the time constant (0.05 m sec, 0.1 m. sec, 1 m.sec amd 10 m. sec and comment on detector output.

**Observation table**

V <sub>m</sub> (input)	Detector Output
1	34.77
2	86.28
3	145.54
4	179.89

V <sub>m</sub> (input)	Time Constant ( R <sub>d</sub> . C <sub>d</sub> )	Detector Output ( describe the ripple)
3m	0.1ms	10.4
3m	1ms	0.307
3m	10ms	0.046

**Conclusion**

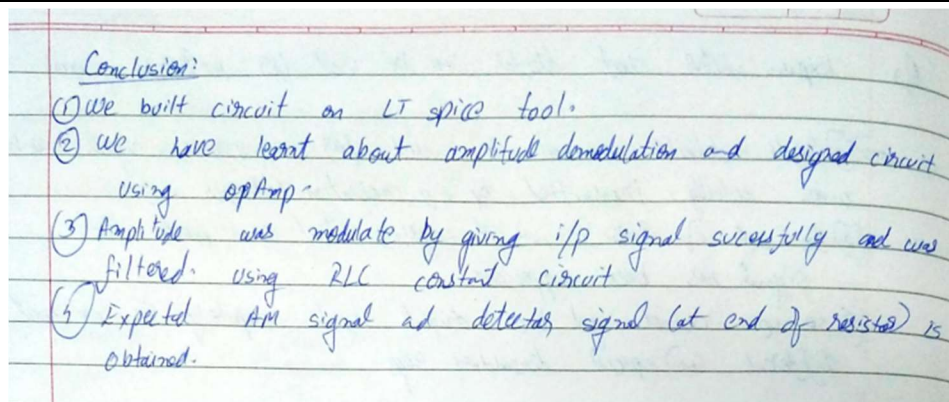

Answer the following Questions.

1. Explain the reason for choppy detector output signal.
2. What happens if RC time constant of detector is too large?
3. Explain whether Diode detector can be used for AM-DSB SC signal



Answer the following

Q1 Explain the reason of choppy detector's o/p signal.

→ (1) Detector signal consist of an ideal diode, capacitor and resistor.

(2) If i/p signal is ~~the~~ <sup>an</sup> ac then the ideal diode is in forward bias, capacitor begins to ~~charge~~ charge upto its peak value and when reaches to peak, AM signal becomes negative. Here diode will be act as open circuit cause of reverse biased mode.

(3) If  $R_c$  is smaller, the capacitor discharges faster through resistor and hence we get choppy detector's o/p signal.

(4) ideal condition if it is  $\frac{1}{f_c} \ll R_c \ll \frac{1}{f_m}$

$f_m$  = max modulating freq.


Q2 what happens if RC time constant of detector is too large?

→ (1) No capacitor charges through diode and internal resistance  $R_s$  when diode is on and discharges through  $R$  when the diode is off


(2) The charging time constant  $R_s C$  should be short as compared to the carrier period  $\frac{1}{f_c}$   $R_s C \ll \frac{1}{f_c}$


(3) Discharging time constant  $R_c$  should be long enough so that the capacitor discharges slowly through load resistance  $R$

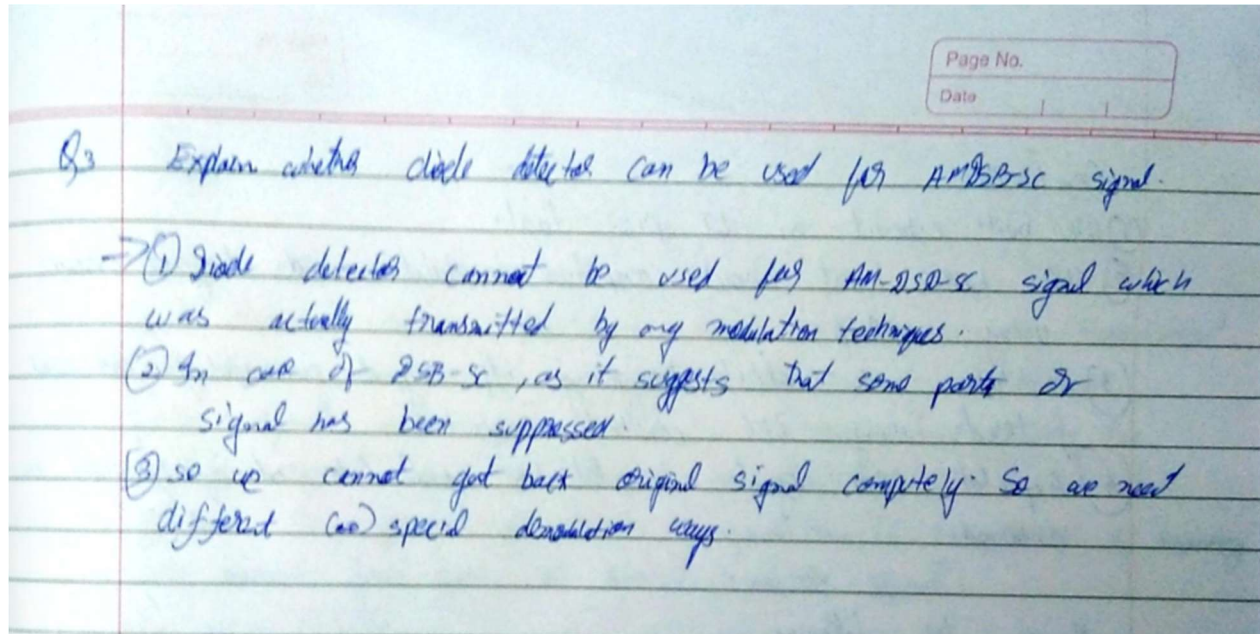(4) But time const should be ~~too~~ long which will not ~~allow~~ allow the capacitor voltage to discharge at the max rate of change of the envelope.  $\therefore \frac{1}{f_c} \ll R_c \ll \frac{1}{f_m}$



## Results:

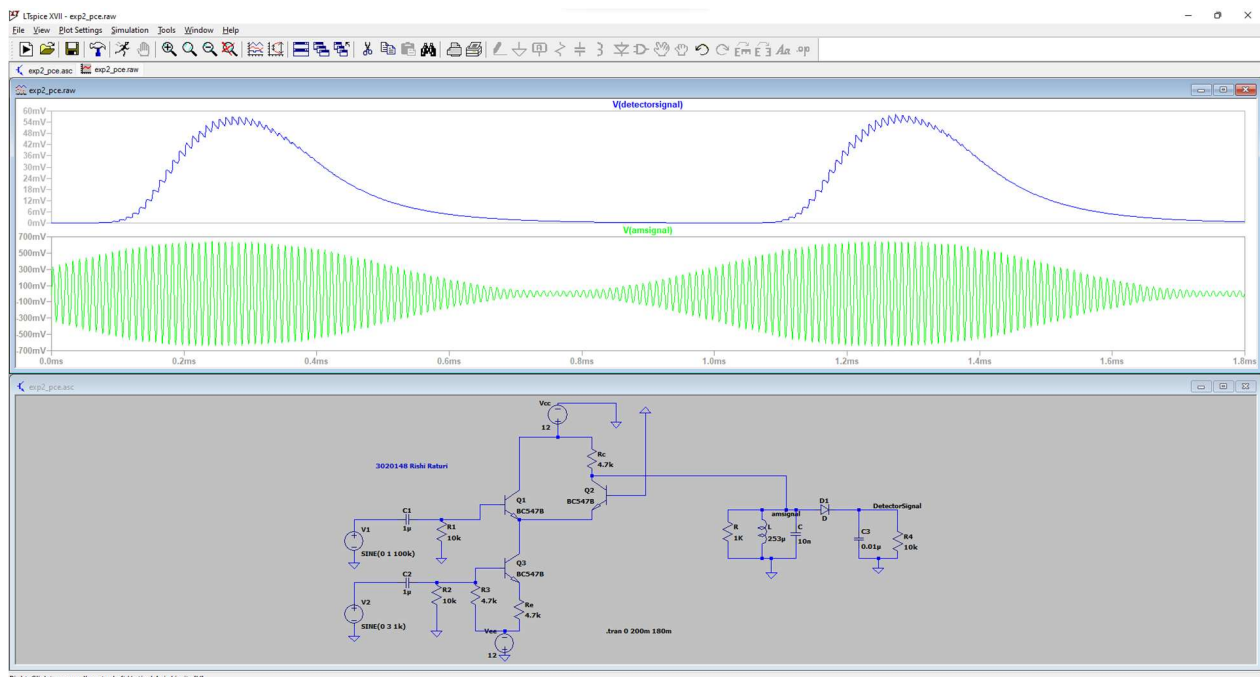

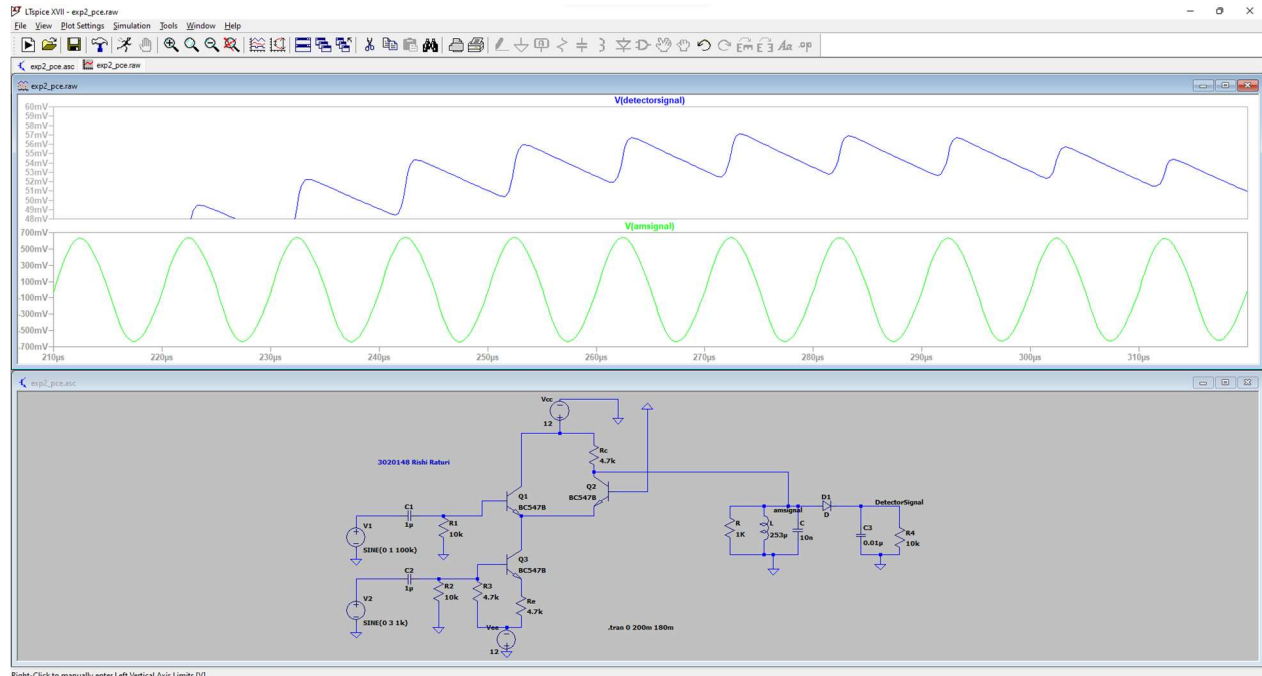

## Circuit Diagram:

